



Circuitos Lógicos ELE15935

PROF. ANSELMO FRIZERA NETO

DEPTO. DE ENGENHARIA ELÉTRICA (UFES)

Lab. 4. Constants and generics

Tópicos da aula de hoje:

- Constants
- Generics

Bibliografia:

- P. Chu, “FPGA Prototyping by VHDL Examples”, Capítulo 3

Constants

Constant values frequently used in expressions and array boundaries

Easier to understand by replacing “hard literals” with symbolic constants


Syntax

- `constant const_name : data_type := value_expression ;`

E.g.,

- `constant DATA_WIDTH : integer := 8;`
- `constant DATA_RANGE : integer := 2** DATA_WIDTH - 1;`

Example: adder with “hard literals”

 

	a ₃	a ₂	a ₁	a ₀
+	b ₃	b ₂	b ₁	b ₀
<hr/>				
cout	sum ₃	sum ₂	sum ₁	sum ₀

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity add_w_carry is
    port (
        a, b : in  std_logic_vector(3 downto 0);
        cout : out std_logic;
        sum  : out std_logic_vector(3 downto 0)
    );
end add_w_carry;
```

```
architecture hard_arch of add_w_carry is
    signal a_ext, b_ext, sum_ext : unsigned(4 downto 0);
begin
    a_ext <= unsigned('0' & a);
    b_ext <= unsigned('0' & b);
    sum_ext <= a_ext + b_ext;
    sum <= std_logic_vector(sum_ext(3 downto 0));
    cout <= sum_ext(4);
end hard_arch;
```

Para “caber” o vai₁ (cout)

Para usar o “+”

} Gera as saídas em std_logic

Example: adder with symbolic constant

```
architecture const_arch of add_w_carry is
    constant N : integer := 4;
    signal a_ext, b_ext, sum_ext : unsigned(N downto 0);
begin
    a_ext    <= unsigned('0' & a);
    b_ext    <= unsigned('0' & b);
    sum_ext  <= a_ext + b_ext;
    sum      <= std_logic_vector(sum_ext(N - 1 downto 0));
    cout     <= sum_ext(N);
end const_arch;
```

Generics

Mechanism to pass info into a component

- Declared in entity declaration
- used as a constant in port declaration and architecture body

Assigned a value when the component is instantiated

The value is fixed after component instantiation

```
entity entity_name is
  generic(
    generic_name: data_type := default_value;
    generic_name: data_type := default_value;
    . . .
    generic_name: data_type := default_value
  )
  port(
    port_name: mode data_type;
    . . .
  );
end entity_name;
```

Adder using a generic

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity gen_add_w_carry is
    generic(N : integer := 4);
    port(
        a, b : in  std_logic_vector(N - 1 downto 0);
        cout : out std_logic;
        sum  : out std_logic_vector(N - 1 downto 0)
    );
end gen_add_w_carry;

architecture arch of gen_add_w_carry is
    signal a_ext, b_ext, sum_ext : unsigned(N downto 0);
begin
    a_ext    <= unsigned('0' & a);
    b_ext    <= unsigned('0' & b);
    sum_ext  <= a_ext + b_ext;
    sum      <= std_logic_vector(sum_ext(N - 1 downto 0));
    cout     <= sum_ext(N);
end arch
```

Example: adder component instantiation

```
signal a4, b4, sum4    : unsigned(3 downto 0);
signal a8, b8, sum8    : unsigned(7 downto 0);
signal a16, b16, sum16: unsigned(15 downto 0);
signal c4, c8, c16     : std_logic;
```

Faltou o entity aqui?

. . .

— *instantiate 8-bit adder*

```
adder_8_unit: work.gen_add_w_carry(arch)
```

```
    generic map(N=>8)
```

```
    port map(a=>a8, b=>b8, cout=>c8, sum=>sum8));
```

— *instantiate 16-bit adder*

```
adder_16_unit: work.gen_add_w_carry(arch)
```

```
    generic map(N=>16)
```



```
    port map(a=>a16, b=>b16, cout=>c16, sum=>sum16));
```

— *instantiate 4-bit adder*

— *(generic mapping omitted, default value 4 used)*

```
adder_4_unit: work.gen_add_w_carry(arch)
```
  
```
    port map(a=>a4, b=>b4, cout=>c4, sum=>sum4));
```





Atividade de hoje

Trabalhando com Display de 7 segmentos

Como funciona o Display de 7 segmentos

N.L. = 0 liga o segmento

 

Representação de sinais hexadecimais




```
library ieee;
use ieee.std_logic_1164.all;
entity hex_to_sseg is
    port(
        hex : in  std_logic_vector(3 downto 0);
        dp  : in  std_logic;
        sseg : out std_logic_vector(7 downto 0)
    );
end hex_to_sseg;

architecture arch of hex_to_sseg is
begin
    with hex select
        sseg(6 downto 0) <=
            "1000000" when "0000",
            "1111001" when "0001",
            "0100100" when "0010",
            "0110000" when "0011",
            "0011001" when "0100",
            "0010010" when "0101",
            "0000010" when "0110",
            "1111000" when "0111",
            "0000000" when "1000",
            "0010000" when "1001",
            "0001000" when "1010", —a
            "0000011" when "1011", —b
            "1000110" when "1100", —c
            "0100001" when "1101", —d
            "0000110" when "1110", —e
            "0001110" when others; —f

        sseg(7) <= dp;
end arch;
```


Displays na Placa Nexys A7

 8 displays de 7 segmentos que funcionam da seguinte forma:



O mesmo sinal de dados vai para todos os displays!
Para mandar dados diferentes para cada display, precisamos de realizar uma varredura dos displays no tempo:
→ **circuito sequencial!**

Escrevendo em vários displays...

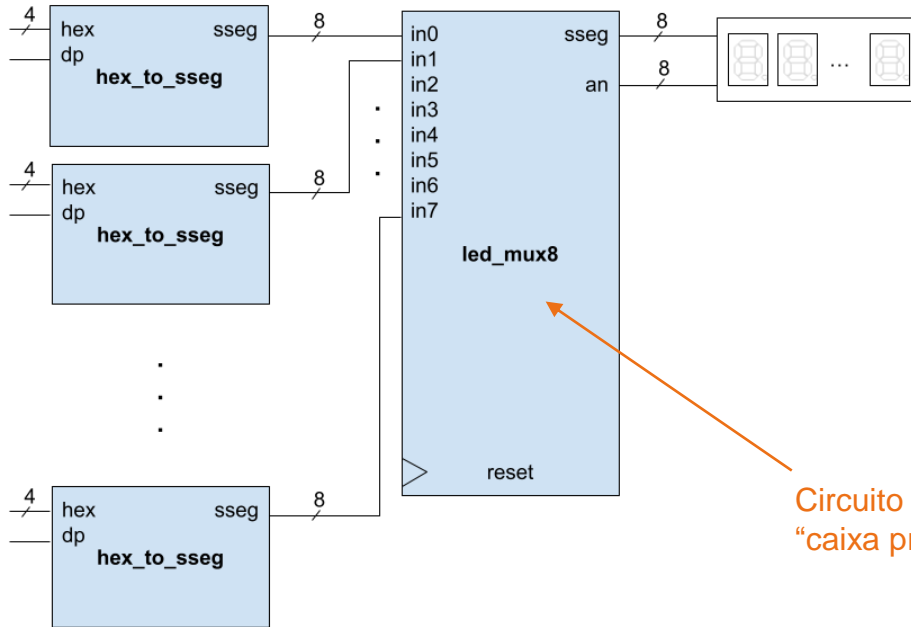

Circuito sequencial!
"caixa preta", por enquanto...

Atividade de hoje

Utilizar os códigos *hex_to_sseg* e *led_mux8* para escrever nos 8 displays:

- Displays 0 e 4 → 0 valor em hexadecimal das chaves sw(3 downto 0)
- Displays 1 e 5 → 0 valor em hexadecimal das chaves sw(7 downto 4)
- Displays 2 e 6 → 0 valor em hexadecimal das chaves sw(11 downto 8)
- Displays 3 e 7 → 0 valor em hexadecimal das chaves sw(15 downto 12)

Desafio:

- Display 0 → 0 valor em hexadecimal das chaves sw(3 downto 0)
- Display 1 → 0 valor em hexadecimal das chaves sw(7 downto 4)
- Display 2 → 0 valor em hexadecimal das chaves sw(11 downto 8)
- Display 3 → 0 valor em hexadecimal das chaves sw(15 downto 12)
- Display 4 → 0 valor em hexadecimal das chaves sw(3 downto 0) + 1
- Display 5 → 0 valor em hexadecimal das chaves sw(7 downto 4) + 1
- Display 6 → 0 valor em hexadecimal das chaves sw(11 downto 8) + 1
- Display 7 → 0 valor em hexadecimal das chaves sw(15 downto 12) + 1